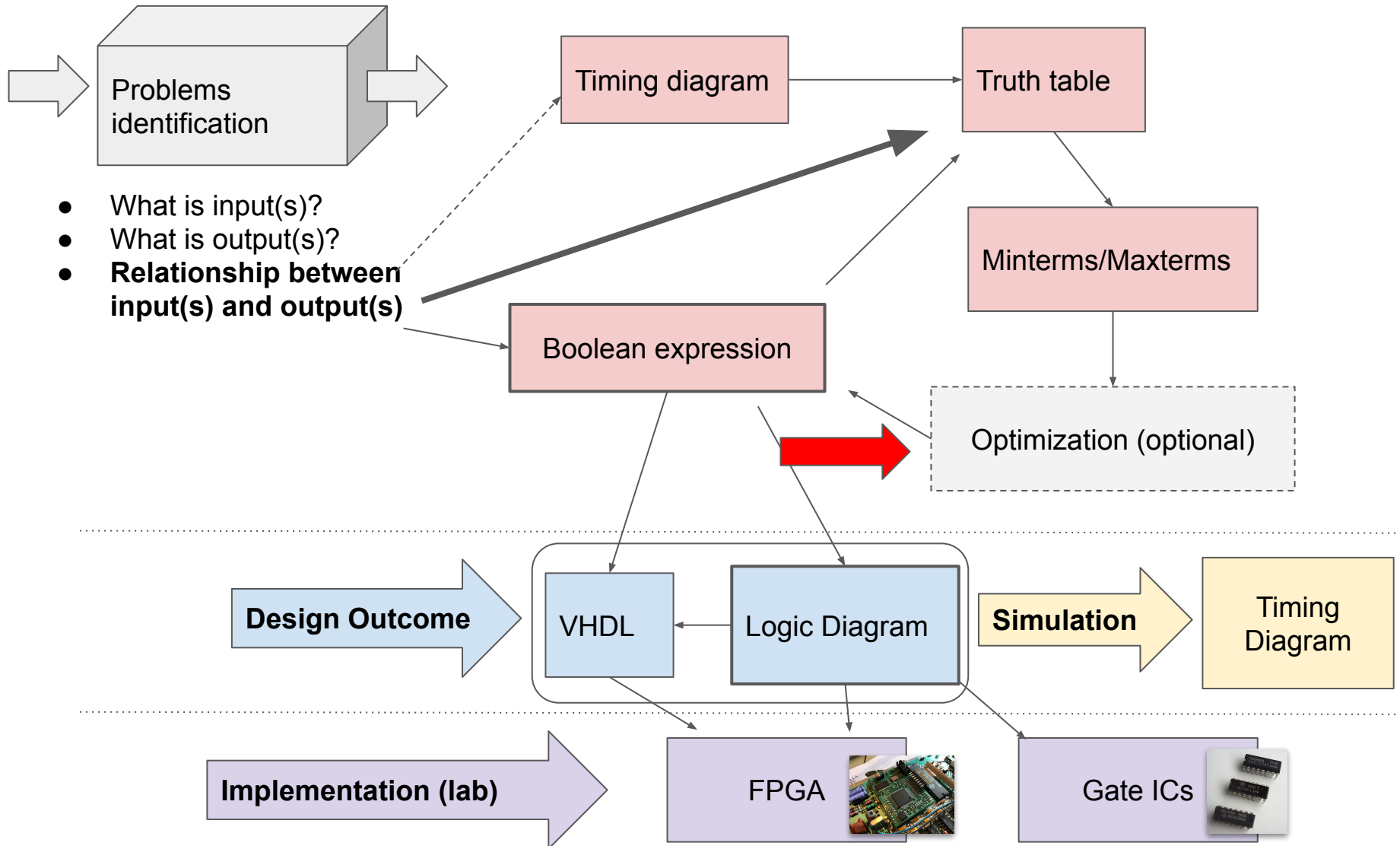


Optimization Implementation of Logic Functions

Chapter 4

Summary of Digital Logic Design



The Map Method

- The complexity of the digital logic gates
 - the complexity of the algebraic expression
- Logic minimization
 - algebraic approaches: lack specific rules
 - the Karnaugh map
 - a simple straightforward procedure
 - a pictorial form of a truth table
 - applicable if the # of variables < 7
 - QM Method (optional)
- A diagram made up of squares
 - each square represents one minterm

Two-Variable Map

- A two-variable map
 - four minterms
 - $x' = \text{row } 0$; $x = \text{row } 1$
 - $y' = \text{column } 0$; $y = \text{column } 1$
 - a truth table in square diagram
 - $xy = m_3$
 - $x+y = \Pi(0) = \Sigma(1, 2, 3)$

m_0	m_1
m_2	m_3

		y	
		0	1
x	0	$x'y'$	$x'y$
	1	xy'	xy

		y	
		0	1
x	0		
	1		1

(a) xy

		y	
		0	1
x	0		1
	1	1	1

(b) $x + y$

A three-variable map

- eight minterms
- the Gray code sequence
 - any two adjacent squares in the map differ by only one variable
 - primed in one square and unprimed in the other
 - e.g., m_5 and m_7 can be simplified
 - $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		y			
		xz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

■ Example 3-1

- $F(x,y,z) = \Sigma(2,3,4,5)$
- $F = x'y + xy'$

xy'

		yz		y		
x		00	01	11	10	
x	0			1	1	$x'y$
	1	1	1			
		z				

- Example 3-2
 - $F(x,y,z) = \sum m(3,4,6,7) = yz + xz'$

		yz		y	
x		0 0	0 1	1 1	1 0
x	0			1	
	1	1		1	1
		z			

■ Four adjacent squares

- 2, 4, 8 and 16 squares

- $m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz'$
 $= x'z'(y' + y) + xz'(y' + y) = x'z' + xz' = z'$

- $m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz$
 $= x'z(y' + y) + xz(y' + y) = x'z + xz = z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		xz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

(b)

- Example 3-3
 - $F(x,y,z) = \Sigma m(0,2,4,5,6)$

Find the optimized logic function

- Prime Implicants
 - all the minterms are covered
 - minimize the number of terms
 - a prime implicant: a product term obtained by combining the maximum possible number of adjacent squares (combining all possible maximum numbers of squares)
 - essential: a minterm is covered by only one prime implicant
 - the **essential PI** must be included

- Example 3-4
 - $F = A'C + A'B + AB'C + BC$

Find the optimized logic function

Four-Variable Map

- The map
 - 16 minterms
 - combinations of 2, 4, 8, and 16 adjacent squares

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

		y			
		yz		11	10
w	wx	00	01		
	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z			

■ Example 3-5

■ $F(w,x,y,z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$

		yz		y	
		0 0	0 1	1 1	1 0
wx	0 0	1	1		1
	0 1	1	1		1
	1 1	1	1		1
	1 0	1	1		
				z	

Diagram illustrating the Karnaugh map for the function $F(w,x,y,z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$. The map is a 4x4 grid with variables w, x, y, z . The rows are labeled wx (00, 01, 11, 10) and the columns are labeled yz (00, 01, 11, 10). The map shows 10 cells containing 1, which correspond to the minterms listed in the function definition. The cells are grouped into three prime implicants: a 2x2 square (minterms 0, 1, 2, 3), a 2x2 square (minterms 4, 5, 6, 7), and a 2x2 square (minterms 8, 9, 12, 13). The prime implicants are circled in blue. The map is also labeled with x and z on the right and bottom respectively.



■ $F = y' + w'z' + xz'$

- Example 3-6
 - $F(A,B,C,D) = ?$

		CD		C	
		00	01	11	10
AB	00	1	1		1
	01				1
	11				
	10	1	1		1
A		B			
		D			

- the simplified expression may not be unique
- $$F = BD + B'D' + CD + AD = BD + B'D' + CD + AB'$$
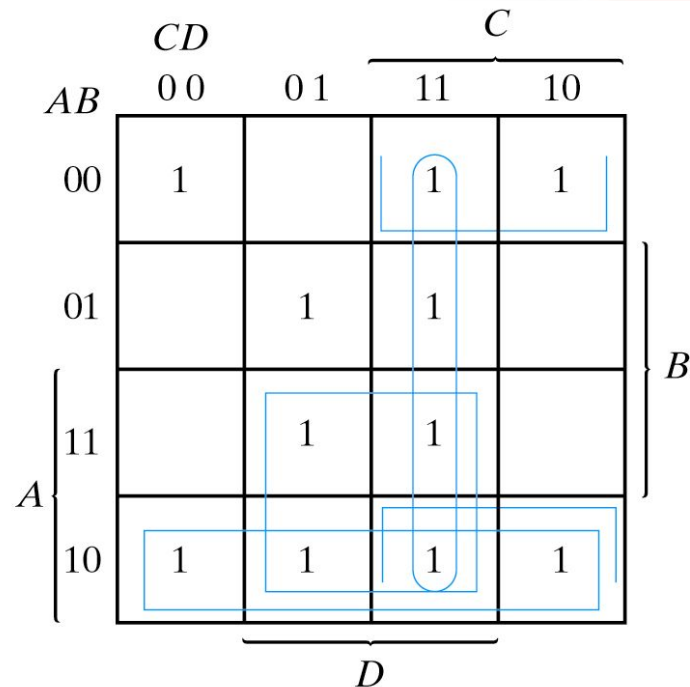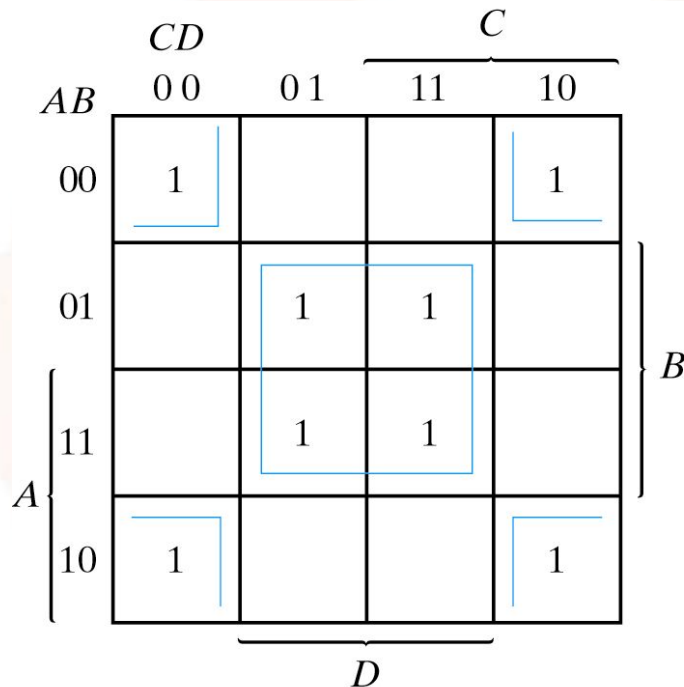
$$= BD + B'D' + B'C + AD = BD + B'D' + B'C + AB'$$



Five-Variable Map

- Map for more than four variables becomes complicated
 - five-variable map: two four-variable map (one on the top of the other)

$A = 0$

		DE		D	
		00	01	11	10
BC	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

E

C

B

$A = 1$

		DE		D	
		00	01	11	10
BC	00	16	17	19	18
	01	20	21	23	22
	11	28	29	31	30
	10	24	25	27	26

E

C

B

■ Example 3-7

■ $F = \Sigma(0,2,4,6,9,13,21,23,25,29,31)$

$A = 0$


	DE		D		
	00	01	11	10	
BC					
00	1			1	}
01	1			1	
11		1			}
10		1			
B					C
	E				

$A = 1$

	DE		D		
	00	01	11	10	
BC					
00					}
01		1	1		
11		1	1		}
10		1			
B					C
	E				

■ $F = A'B'E' + BD'E + ACE$

Six-Variable Map

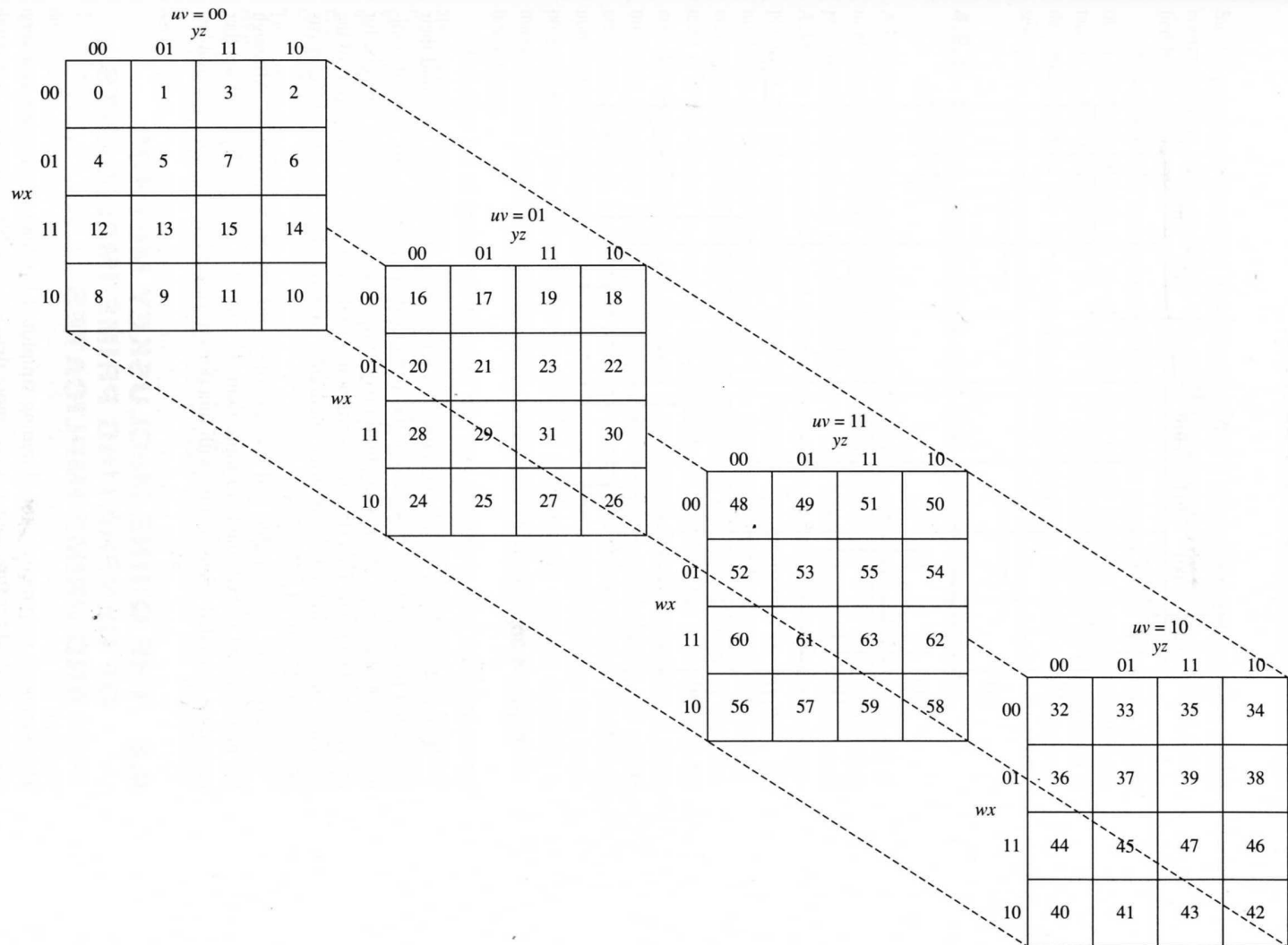

(b)

Product of Sums Simplification

- Approach #1
 - Simplified F' in the form of sum of products
 - Apply DeMorgan's theorem $F = (F')'$
 - F' : sum of products $\Rightarrow F$: product of sums
- Approach #2: duality
 - combinations of maxterms (it was minterms)
 - $M_0 M_1 = (A+B+C+D)(A+B+C+D')$ $_{CD}$ =

$$(A+B+C)+(DD')=A+B+C$$

AB	00	01	11	10
00	M_0	M_1	M_3	M_2
01	M_4	M_5	M_7	M_6
11	M_{12}	M_{13}	M_{15}	M_{14}
10	M_8	M_9	M_{11}	M_{10}

■ Example 3-8

■ $F = \Sigma(0,1,2,5,8,9,10)$

		<i>CD</i>		<i>C</i>	
		00	01	11	10
<i>AB</i>	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

Diagram illustrating a 4x4 Karnaugh map for the function $F = \Sigma(0,1,2,5,8,9,10)$. The map is labeled with *AB* on the vertical axis and *CD* on the horizontal axis. The map shows the following values:

- Row 00: 1, 1, 0, 1
- Row 01: 0, 1, 0, 0
- Row 11: 0, 0, 0, 0
- Row 10: 1, 1, 0, 1

The map is grouped into four regions, each labeled with a letter and a bracket:


- A*: Groups the first two rows (00 and 01).
- B*: Groups the last two rows (11 and 10).
- C*: Groups the first two columns (00 and 01).
- D*: Groups the last two columns (11 and 10).

■ $F' = AB + CD + BD'$


■ Apply DeMorgan's theorem; $F = (A' + B')(C' + D')(B' + D)$

■ Or think in terms of maxterms

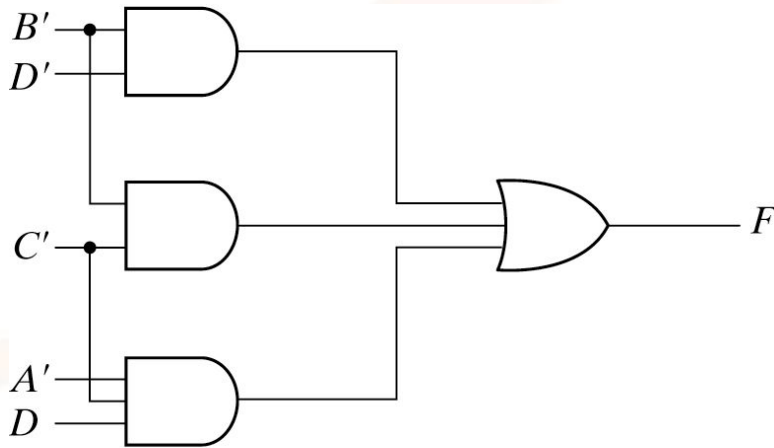■ Gate implementation of the function of Example 3-8



(a) $F = B'D' + B'C' + A'C'D$

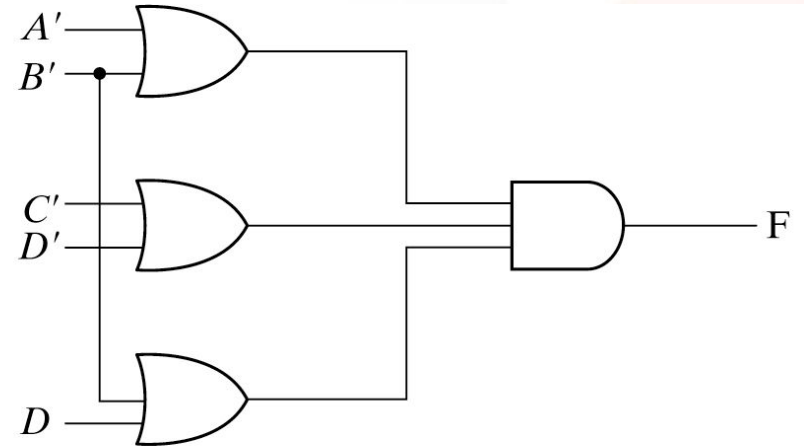

(b) $F = (A' + B')(C' + D')(B' + D)$

Don't-Care Conditions

- The value of a function is not specified for certain combinations of variables
 - BCD; 1010-1111: don't care
- The don't care conditions can be utilized in logic minimization
 - can be implemented as 0 or 1
- Example 3-9
 - $F(w,x,y,z) = \Sigma(1,3,7,11,15)$
 - $d(w,x,y,z) = \Sigma(0,2,5)$

- $F = yz + w'x'$; $F = yz + w'z$
- $F = \Sigma(0,1,2,3,7,11,15)$; $F = \Sigma(1,3,5,7,11,15)$
- either expression is acceptable




		yz		y	
		00	01	11	10
wx	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			
w		x			

		yz		y	
		00	01	11	10
wx	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			
w		x			


- Also apply to products of sum

NAND and NOR Implementation

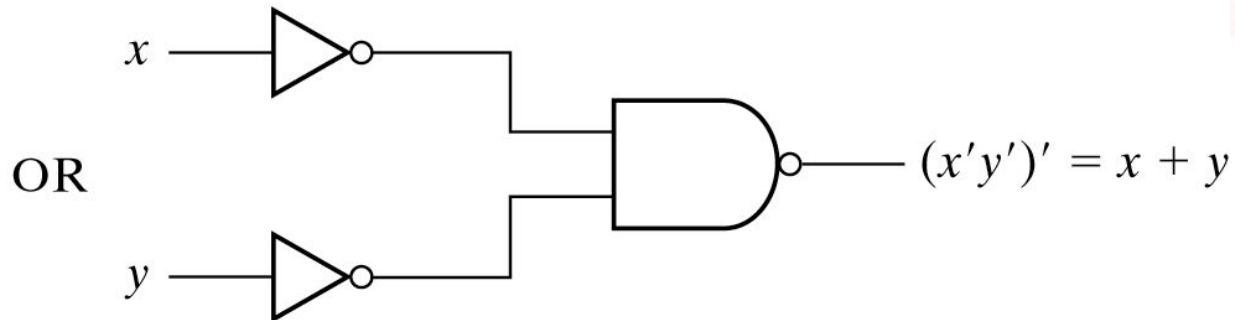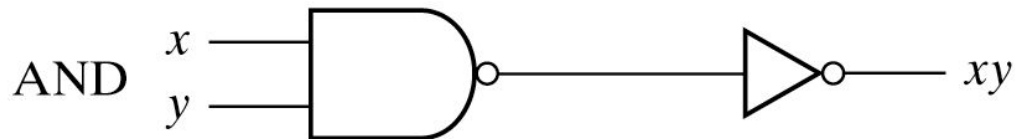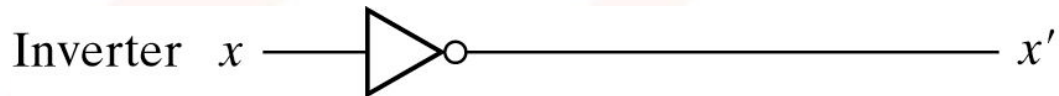
- NAND gate is a universal gate
 - can implement any digital system



- Two graphic symbols for a NAND gate

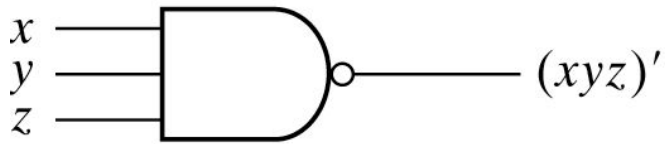


(a) AND-invert

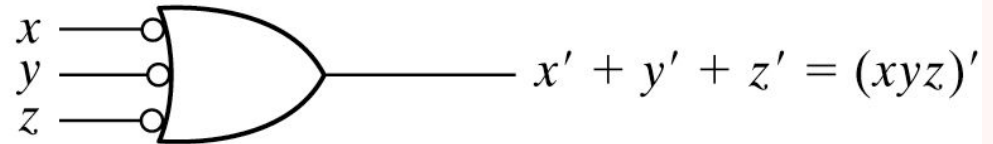

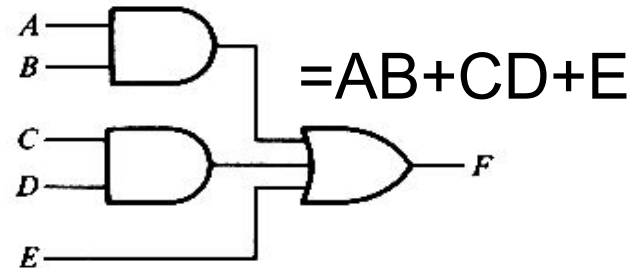
(b) Invert-OR

Two-level Implementation


- two-level logic
- NAND-NAND = sum of products
- Example: $F = AB + CD + E$
- $F = ((AB)' (CD)' E')'$



(a) AND-OR

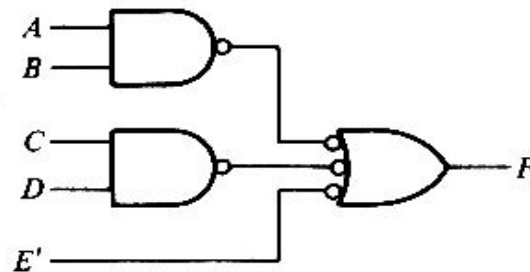


(b) NAND-NAND

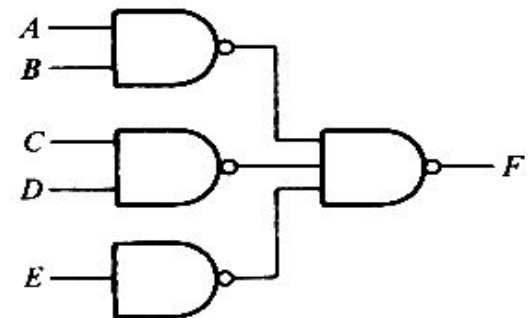


(c) NAND-NAND


■ $F = AB + CD$

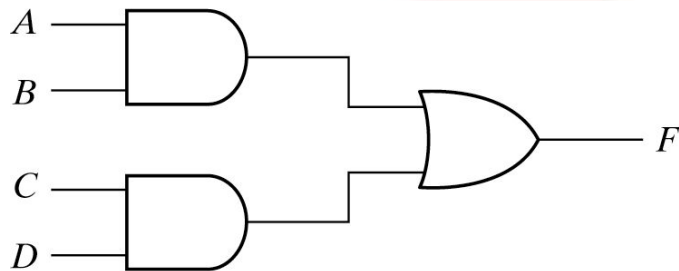

(a)

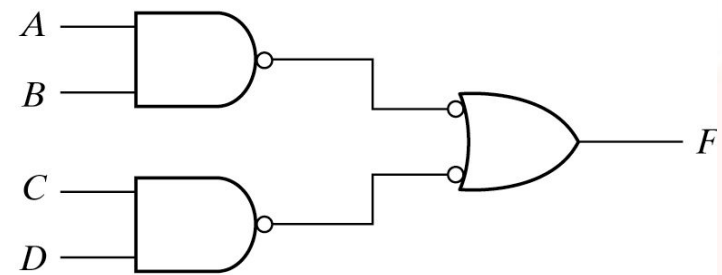

(b)

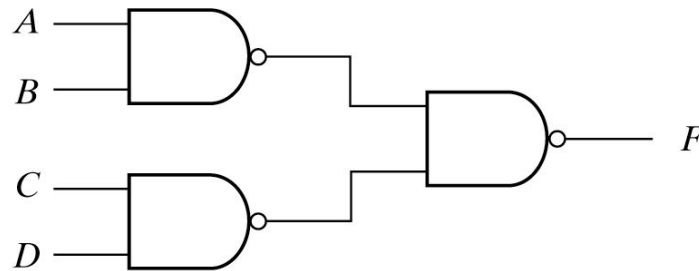


(c)


Fig. 3-20 Three Ways to Implement $F = AB + CD$

- The procedure for NAND-NAND implementation
 - simplified in the form of sum of products
 - a NAND gate for each product term; the inputs to each NAND gate are the literals of the term
 - a single NAND gate for the second sum term


■ Example 3-10

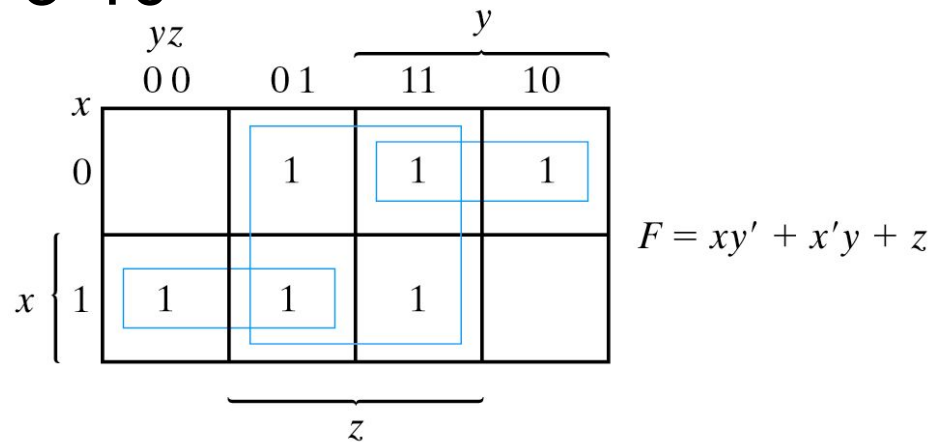

(a)

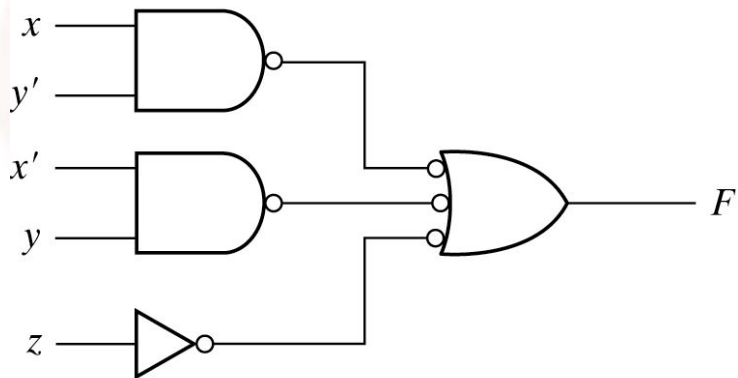




(b)

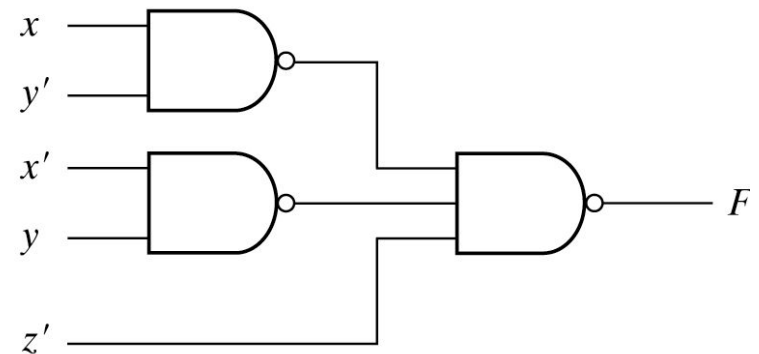


(c)

NOR Implementation

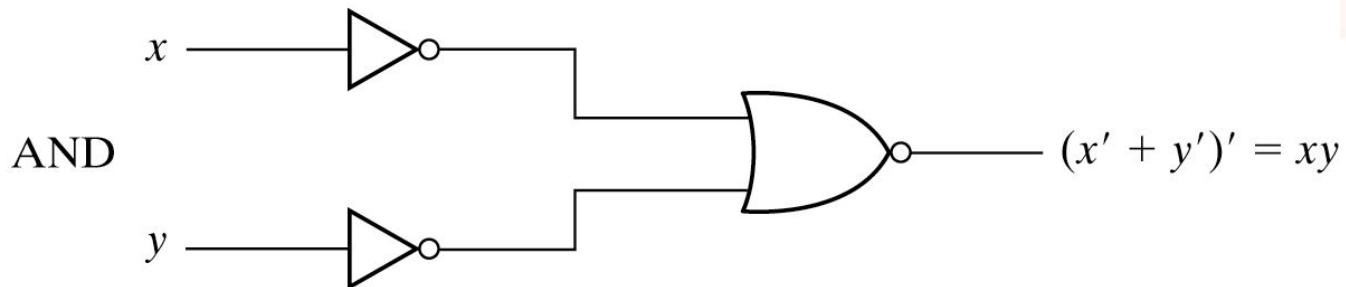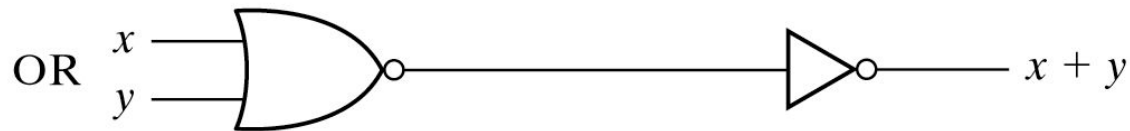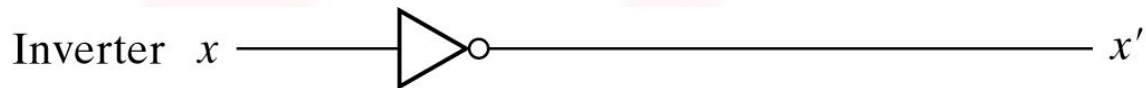
- NOR function is the dual of NAND function
- The NOR gate is also universal



- Two graphic symbols for a NOR gate

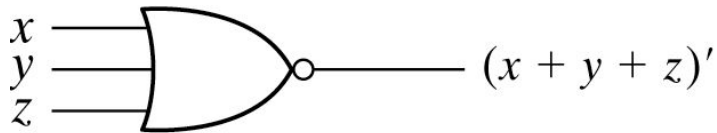


(a) OR–invert

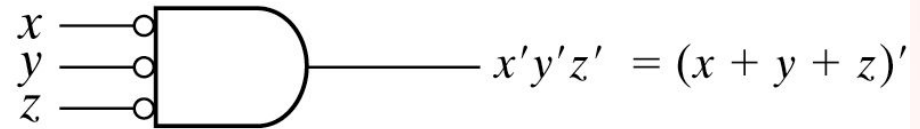

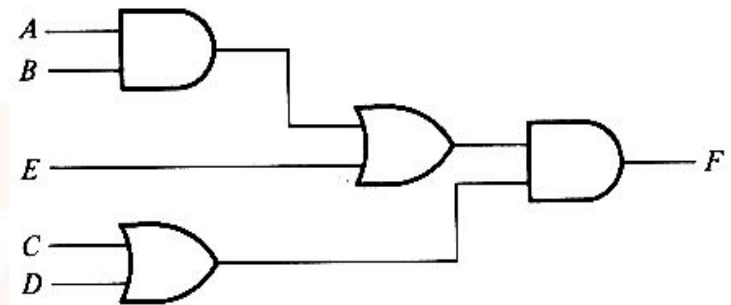
(a) Invert–AND

■ Boolean-function implementation


- OR \Rightarrow NOR + INV
- AND
 - INV + AND = NOR



(a) AND-OR diagram

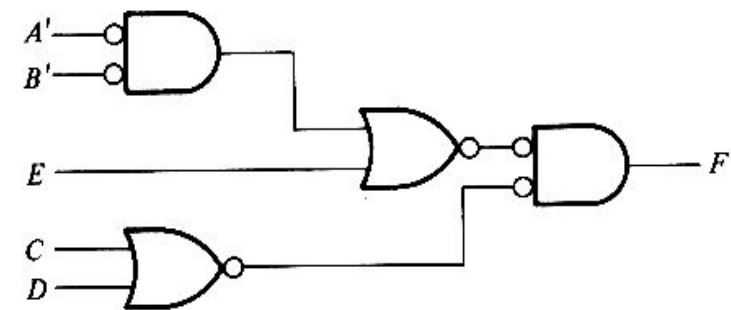

(b) NOR diagram

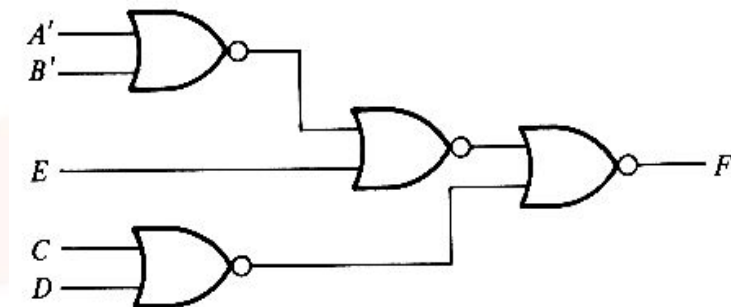


(c) Alternate NOR diagram

Other two level implementations


- 16 possible combinations of two-level forms
 - eight of them: degenerate forms = a single operation
 - AND-AND, OR-OR, AND-NAND, OR-NOR, NAND-OR, NOR-AND, NOR-NAND, NAND-NOR
 - The eight non degenerate forms
 - AND-OR, OR-AND, NAND-NAND, NOR-NOR, NOR-OR, NAND-AND, OR-NAND, AND-NOR
 - AND-OR and NAND-NAND = sum of products
 - OR-AND and NOR-NOR = product of sums
 - NOR-OR, NAND-AND, OR-NAND, AND-NOR = ?

AND-OR-Invert Implementation

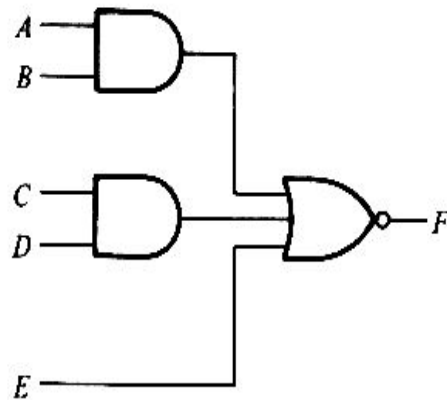
- AND-OR-INVERT (AOI) Implementation
 - NAND-AND = AND-NOR = AOI
 - $F = (AB + CD + E)'$
 - $F' = AB + CD + E$ (sum of products)



(a) AND-NOR

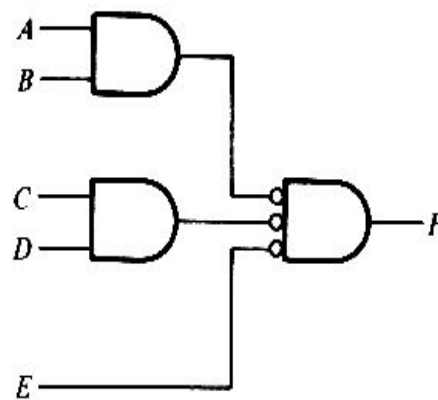


(b) AND-NOR

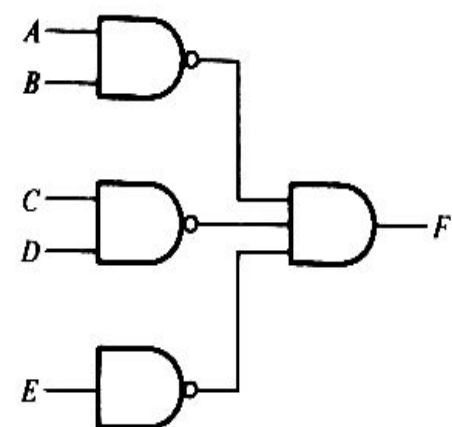

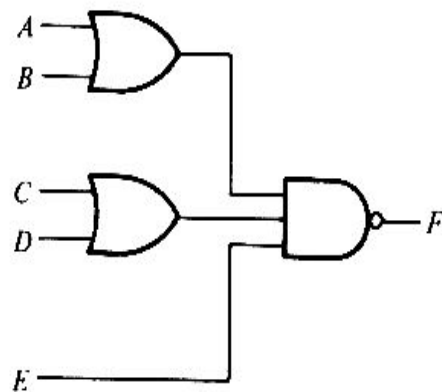
(c) NAND-AND

- simplify F' in sum of products


- OR-AND-INVERT (OAI) Implementation
 - OR-NAND = NOR-OR = OAI
 - $F = ((A+B)(C+D)E)'$
 - $F' = (A+B)(C+D)E$ (product of sums)



(a) OR-NAND

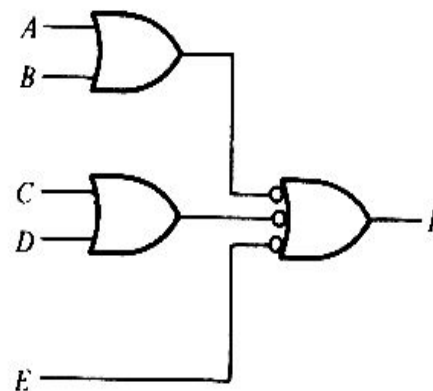

(b) OR-NAND

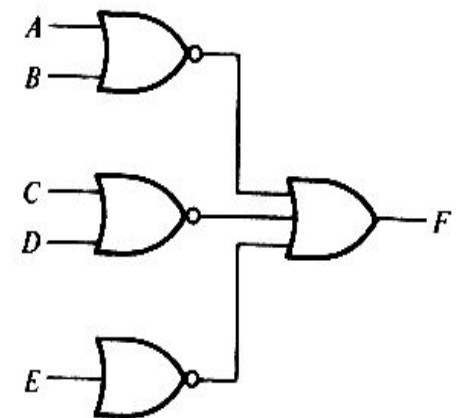

(c) NOR-OR

- simplified F' in products of sum

■ Example 3-11

- $F' = x'y + xy' + z$ (F' : sum of products)
- $F = (x'y + xy' + z)'$ (F : AOI implementation)

- $F = x'y'z' + xyz'$ (F : sum of products)
- $F' = (x + y + z)(x' + y' + z)$ (F' : product of sums)
- $F = ((x + y + z)(x' + y' + z))'$ (F : OAI)


		yz		y	
		00	01	11	10
x	0	1	0	0	0
	1	0	0	0	1

z


$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

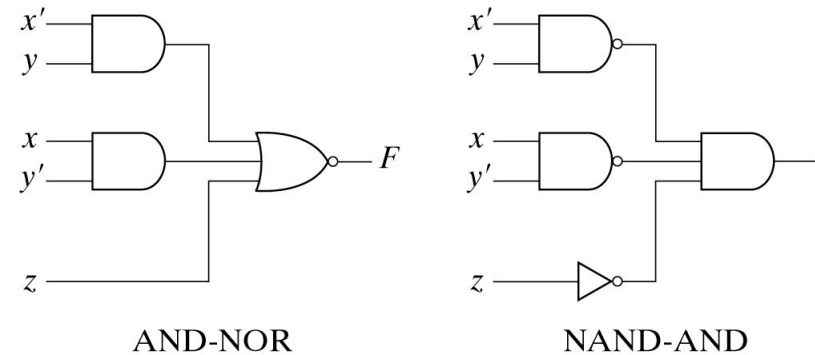(a) Map simplification in sum of products.



(b) $F = (x'y + xy' + z)'$

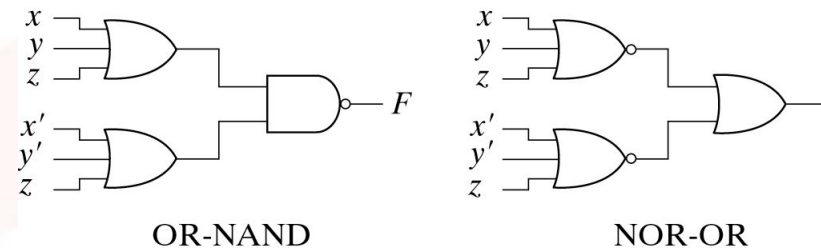


(c) $F = [(x + y + z)(x' + y' + z)]'$

Exclusive-OR Function


- Exclusive-OR (XOR)
 - $x \oplus y = xy' + x'y$
- Exclusive-NOR (XNOR)
 - $(x \oplus y)' = xy + x'y'$
- Some identities
 - $x \oplus 0 = x$
 - $x \oplus 1 = x'$
 - $x \oplus x = 0$
 - $x \oplus x' = 1$
 - $x \oplus y' = (x \oplus y)'$
 - $x' \oplus y = (x \oplus y)'$
- Commutative and associative
 - $A \oplus B = B \oplus A$
 - $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

■ Implementations

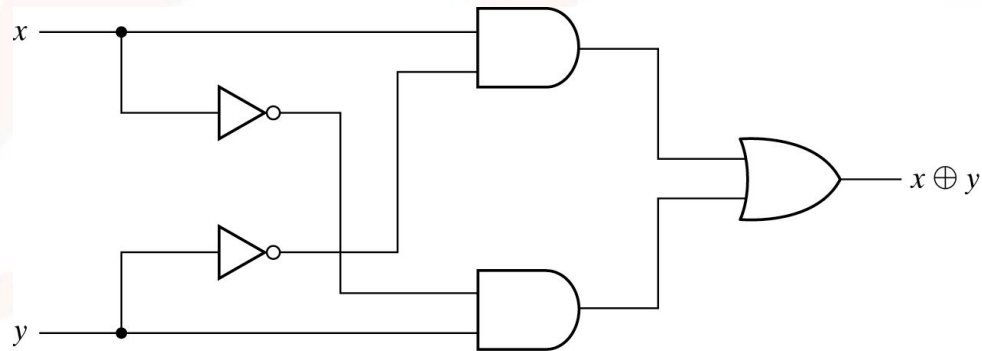- $(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$



(a) With AND-OR-NOT gates

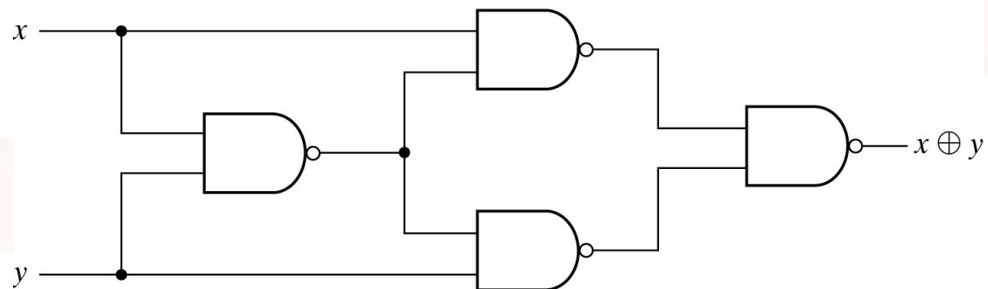

(b) With NAND gates

Odd and Even functions

- $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C$
- $= AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$
- an odd number of 1's

		BC		B	
		00	01	11	10
A	0		1		1
	1	1		1	

C


(a) Odd function
 $F = A \oplus B \oplus C$

		BC		B	
		00	01	11	10
A	0	1		1	
	1		1		1


C

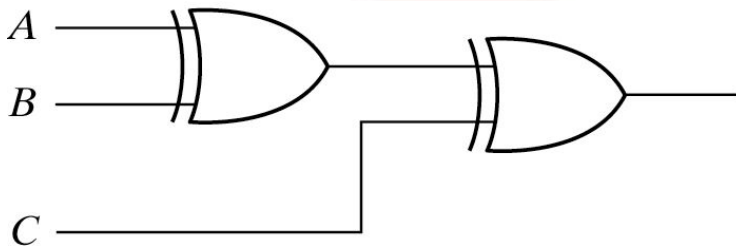(a) Even function
 $F = (A \oplus B \oplus C)'$

- Logic diagram of odd and even functions



(a) 3-input odd function

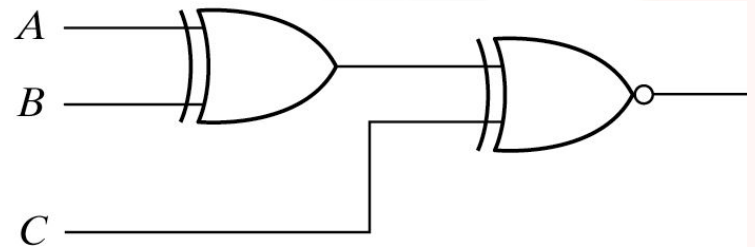

(b) 3-input even function

■ Four-variable Exclusive-OR function

$$\begin{aligned} \blacksquare A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) \\ &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D) \end{aligned}$$

		CD		C		
		00	01	11	10	
AB	00		1		1	B
	01	1		1		
	11		1		1	
	10	1		1		
		D				


(a) Odd function
 $F = A \oplus B \oplus C \oplus D$

		CD		C		
		00	01	11	10	
AB	00	1		1		B
	01		1		1	
	11	1		1		
	10		1		1	
		D				

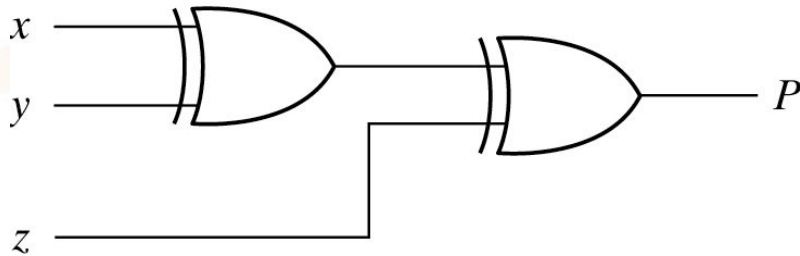
(b) Even function
 $F = (A \oplus B \oplus C \oplus D)'$

Parity Generation and Checking

- Parity Generation and Checking
 - a parity bit: $P = x \oplus y \oplus z$
 - parity check: $C = x \oplus y \oplus z \oplus P$
 - $C=1$: an odd number of data bit error
 - $C=0$: correct or an even # of data bit error



(a) 3-bit even parity generator

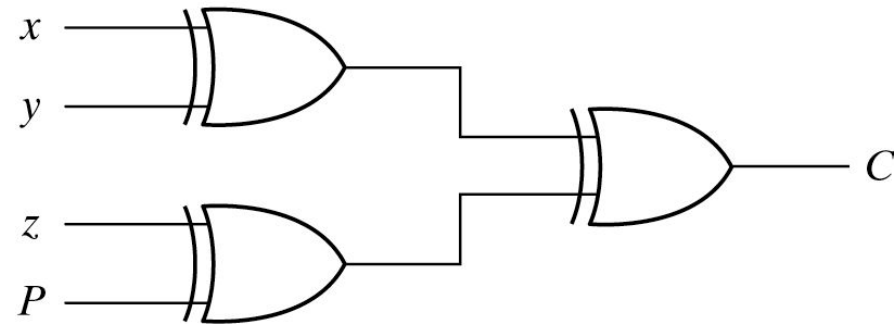

(a) 4-bit even parity checker