

# Digital Circuits and Logic Design

## Lecture6-2 :Number Representation and Arithmetic Circuits

# Note: Half-Adder (HA)



$$\begin{array}{r}
 x \\
 + y \\
 \hline
 c \ s
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0 \ 0
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 0 \ 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 0 \ 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 1 \ 0
 \end{array}$$



(a) The four possible cases

		Carry	Sum
$x$	$y$	$c$	$s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

  

# Note: Full-Adder (FA)

Addition at the i-th bit:

$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

# Note: Full-Adder (FA)


$x_i y_i$ $c_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$x_i y_i$ $c_i$	00	01	11	10
0			1	
1		1	1	1


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 


(c) Circuit
 
# Note: Alternative Implementation of Adder



(a) Block diagram

 

(b) Detailed diagram

Figure 5.5. A decomposed implementation of the full-adder circuit.

# Note: Ripple Carry Adder


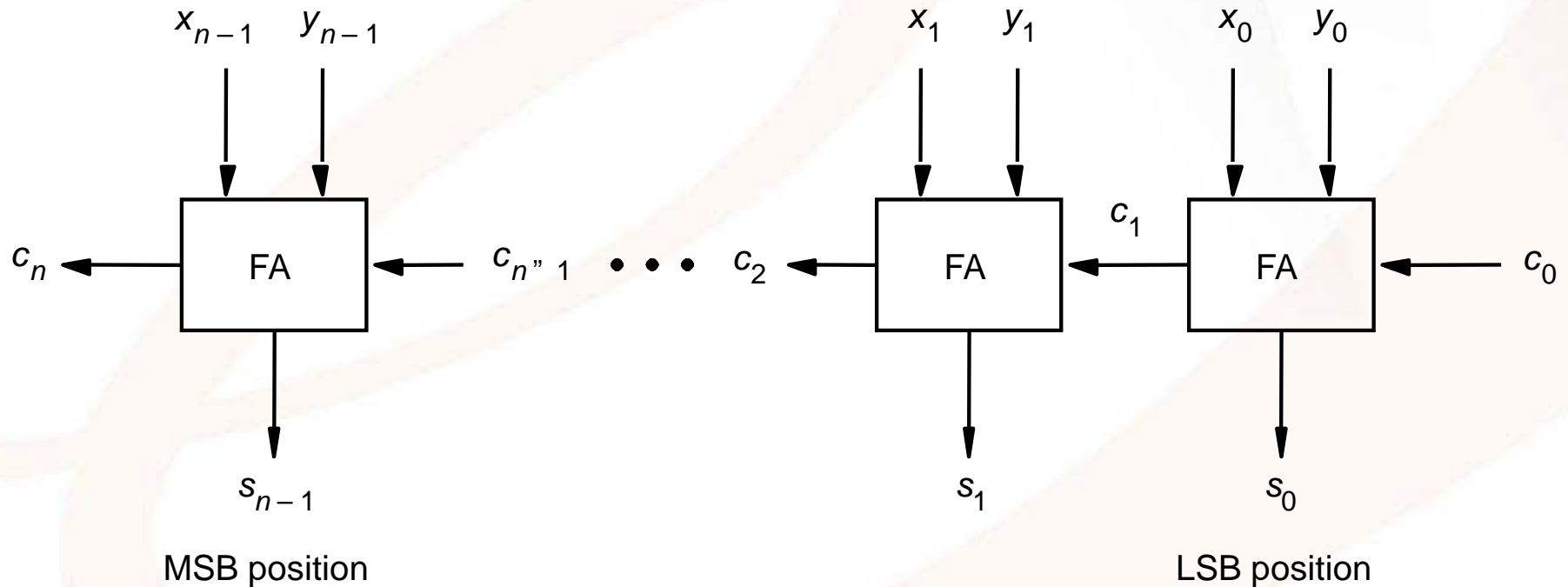


Figure 5.6. An  $n$ -bit ripple-carry adder.

# Note: Adder/subtractor unit.

 

# Carry-lookahead adder

$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Recall the carry-out function for stage I can be realized as

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

$$\underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

**generate propagate**

$$c_{i+1} = g_i + p_i c_i$$



# Carry-lookahead adder

- The function  $g_i=1$  when both  $x_i$  and  $y_i$  are 1, regardless of the incoming carry  $c_i$ 
  - Since in this case, stage  $i$  is guaranteed to generate a carry-out,  $g$  is called the **generate** function

$$C_{i+1} = g_i + p_i c_i$$

$$g_i = x_i y_i$$

$$1 = 1 + d$$

**generate**

Carry-Out = 1 if (g=1)

$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Carry-lookahead adder

- The function  $p_i=1$  when either  $x_i$  and  $y_i$  are 1  
A carry-out is produced if  $c_i=1$ 
  - The effect is that the carry-in of 1 is propagated through stage  $i$ ;  $p$  is called the **propagate** function

$$c_{i+1} = g_i + p_i c_i$$

$p_i = x_i + y_i$   
 $c_i = 1$   
 $1 = 1 + 1$   
**propagate**

$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Carry-Out  $\leq$  (Carry-In of 1) if ( $p=1$ )

# Carry-lookahead adder

## Why Generate and Propagate?

Why generate and propagate. If you look at the Boolean expressions for  $p_i$  and  $g_i$ , you will see that they both use only  $x_i$  and  $y_i$ . Neither depend on the carry. Since  $x_i$  and  $y_i$  are available immediately, this gives us hope that we can avoid waiting for carries.

## Carry-lookahead adder

First, let's write the  $c_1$  which is the carry out for the adding bit 0 of  $x$  and  $y$ .

$$c_1 = g_0 + p_0 c_0$$

Now, we write it for  $c_2$ .

$$c_2 = g_1 + p_1 c_1$$

$$\begin{aligned} c_2 &= g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

## Carry-lookahead adder

Let's go one more step further:

$$\begin{aligned}c_3 &= g_2 + p_2 c_2 \\&= g_2 + p_2(g_1 + p_1 g_0 + p_1 p_0 c_0) \\&= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0\end{aligned}$$

Already, you should be able to detect a pattern.  
By following the same pattern, you'd expect:

$$**c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0**$$

# Carry-lookahead (CLA) adder

carry generated in stage  $n-2$ , and propagated through remaining stages

carry generated in stage 0, and propagated through remaining stages

$$c_n = g_{n-1} + p_{n-1}g_{n-2} + p_{n-1}p_{n-2}g_{n-3} + \dots + p_{n-1}p_{n-2}\dots p_1g_0 + p_{n-1}p_{n-2}\dots p_0c_0$$

carry generated in last stage


carry generated in stage  $n-3$ , and propagated through remaining stages

Input carry  $c_0$  propagated through all stages

## n-bit Adder

# Ripple-Carry adder


## 4-bit ripple-carry adder

 

Main Delay Time – wait for carry bit in each FA blocks

# Carry-lookahead (CLA) adder

## 4-bit carry-Lookahead adder

 

Main Delay Time Decrease – We don't have to wait for carry bit in each FA blocks. But we're able to compute the carries in terms of  $x_i$ ,  $y_i$ , and  $c_0$ .



# Ripple-carry adder critical path



3 gate delays for  $c_1$ ,  
5 gate delays for  $c_2$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

$$g_i = x_i y_i$$

$$p_i = x_i + y_i$$

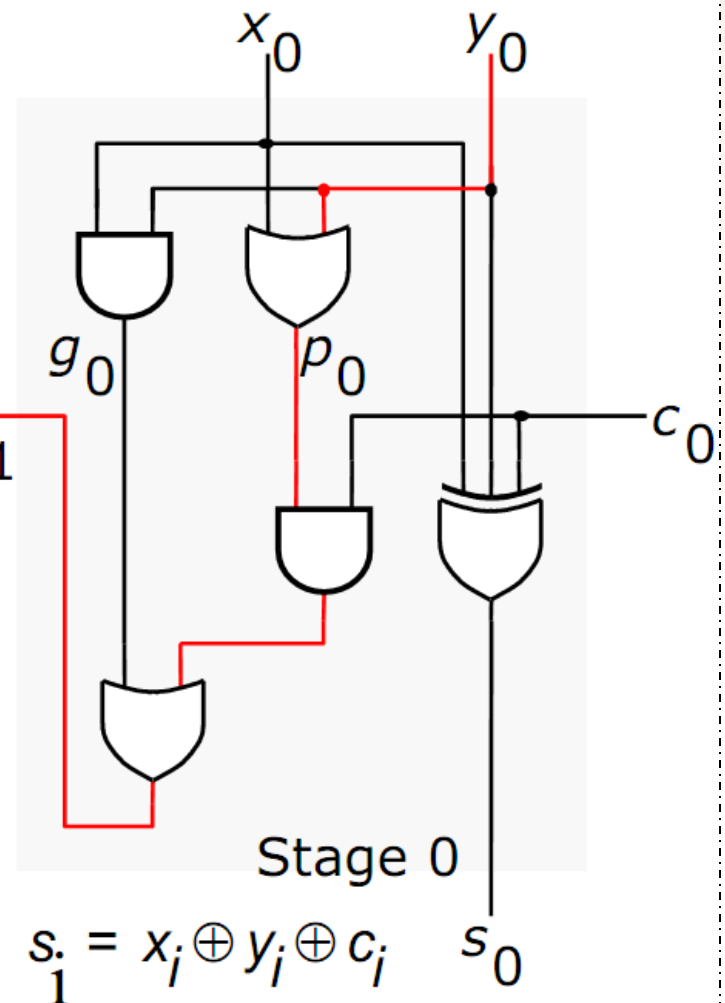 In general,  $2n+1$  delays  
for  $n$ -bit ripple-carry adder



# Carry-lookahead critical path

3 gate delays for  $c_1$ ,  
3 gate delays for  $c_2$   
3 gate delays for  $c_n$

$$c_{i+1} = g_i + p_i c_i$$

$$g_i = x_i y_i$$


$$p_i = x_i + y_i$$

Total delay for  $n$ -bit  
CLA adder is 4 gate  
delays

All  $g_i$  and  $p_i$ , one delay

All  $c_i$ , two more delays

One more delay for the  
sums  $s_i$

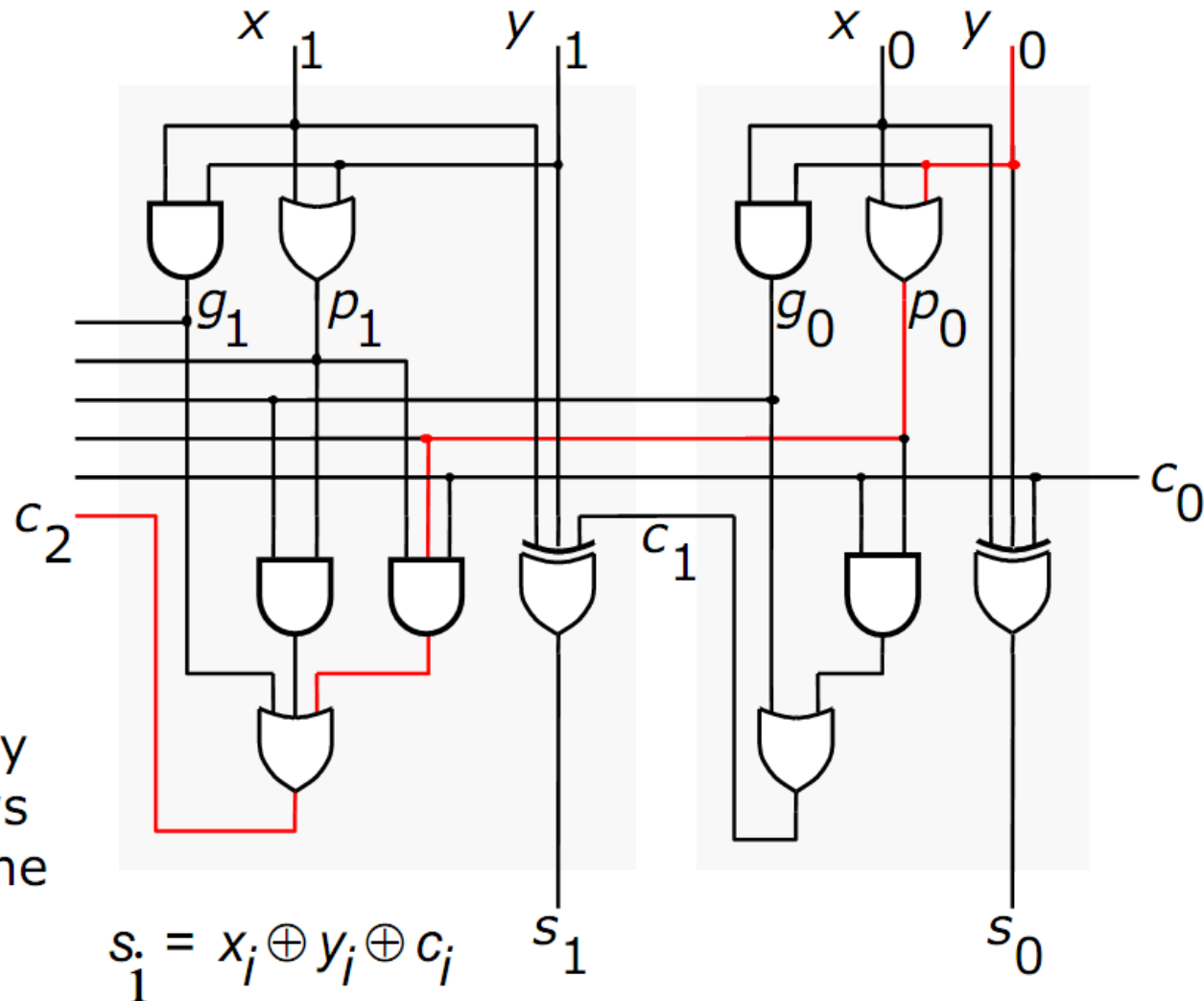

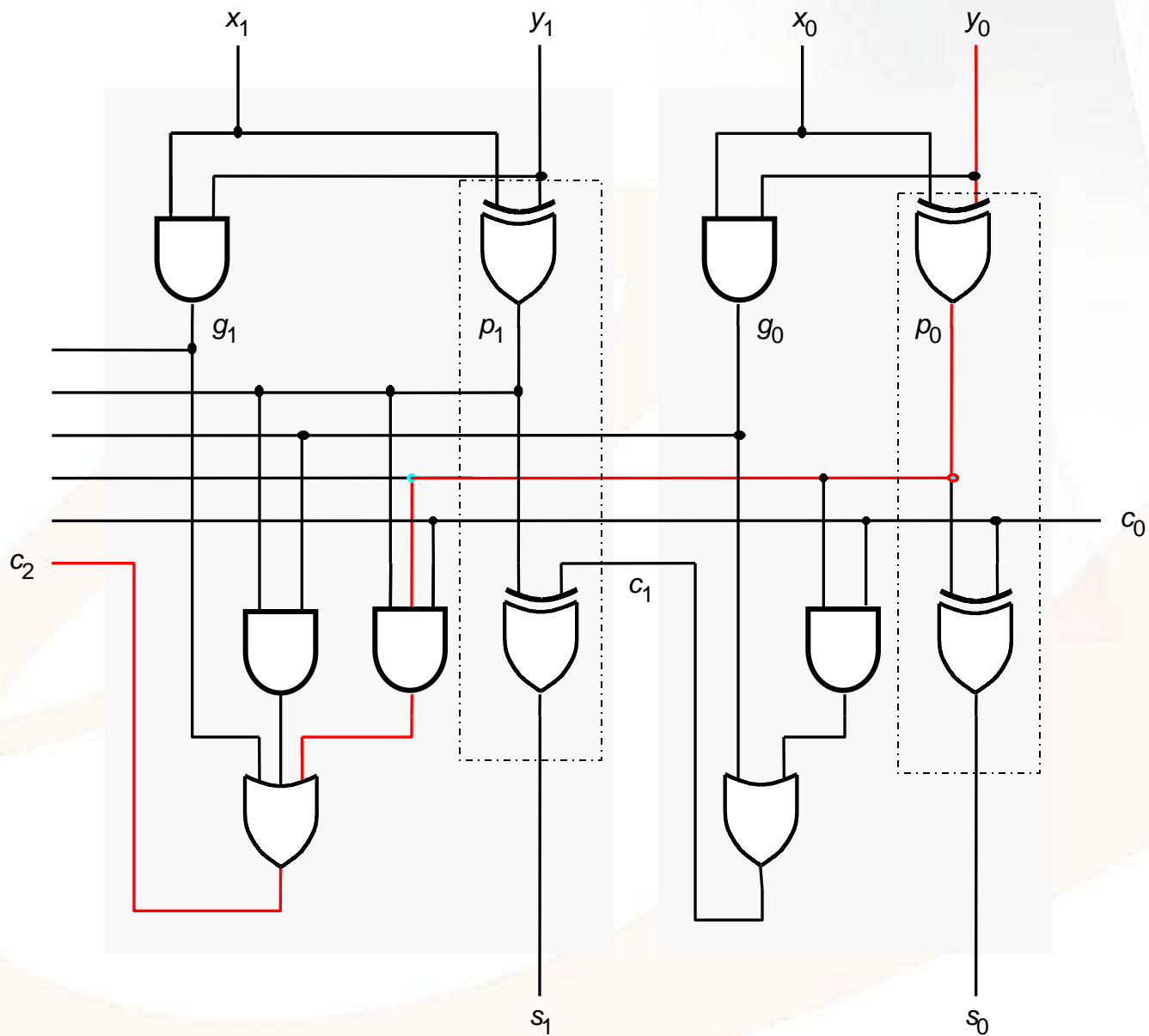


Figure 5.19. An alternative design for a carry-lookahead adder.

# Carry-lookahead limitations

- The expression for carry in a CLA adder


$$c_n = g_{n-1} + p_{n-1}g_{n-2} + p_{n-1}p_{n-2}g_{n-3} + \dots + p_{n-1}p_{n-2}\dots p_1g_0 + p_{n-1}p_{n-2}\dots p_0c_0$$

- obviously results in a fast solution (since it is only a 2 level AND-OR function)
- Fan-in limitations may effectively limit the speed of a CLA adder
  - Devices with known fan-in limitations (such as an FPGA) often include dedicated circuitry for implementation of fast adders
- The complexity of an  $n$ -bit CLA adder increases rapidly as  $n$  becomes large
  - To reduce this complexity, we can use a *hierarchical* approach in designing large adders


# 32-bit adder design

- Suppose we want to design a 32-bit adder
- Divide this adder into 4 blocks such that
  - Bits  $b_{7-0}$  are block 0
  - Bits  $b_{15-8}$  are block 1
  - Bits  $b_{23-16}$  are block 2
  - Bits  $b_{31-24}$  are block 3
- Each block can be constructed as an 8-bit CLA adder
  - The carry-out signals from the four blocks are  $c_8$ ,  $c_{16}$ ,  $c_{24}$ , and  $c_{32}$
- There are 2 basic approaches for interconnecting these four blocks
  - Ripple-carry between blocks
  - Second level carry-lookahead circuit

# Ripple-carry between blocks

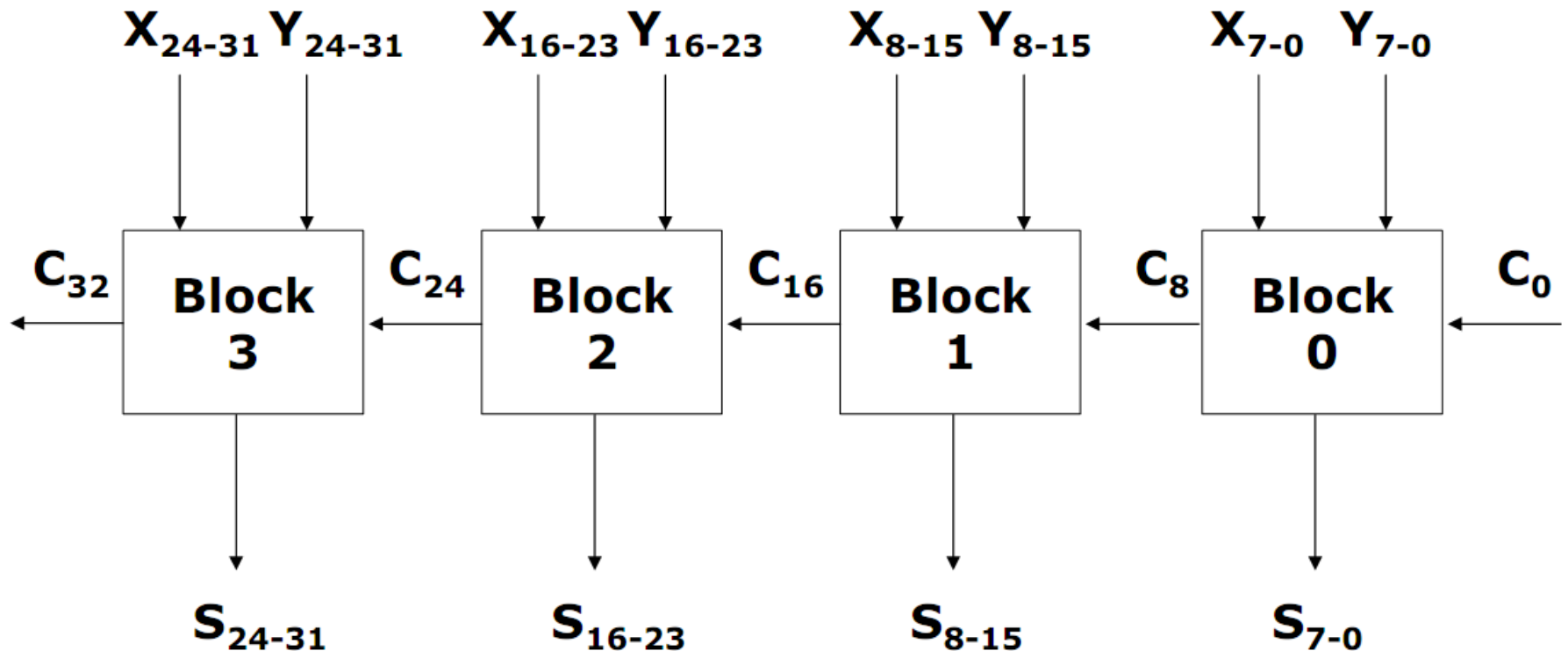

# Second level carry-lookahead circuit

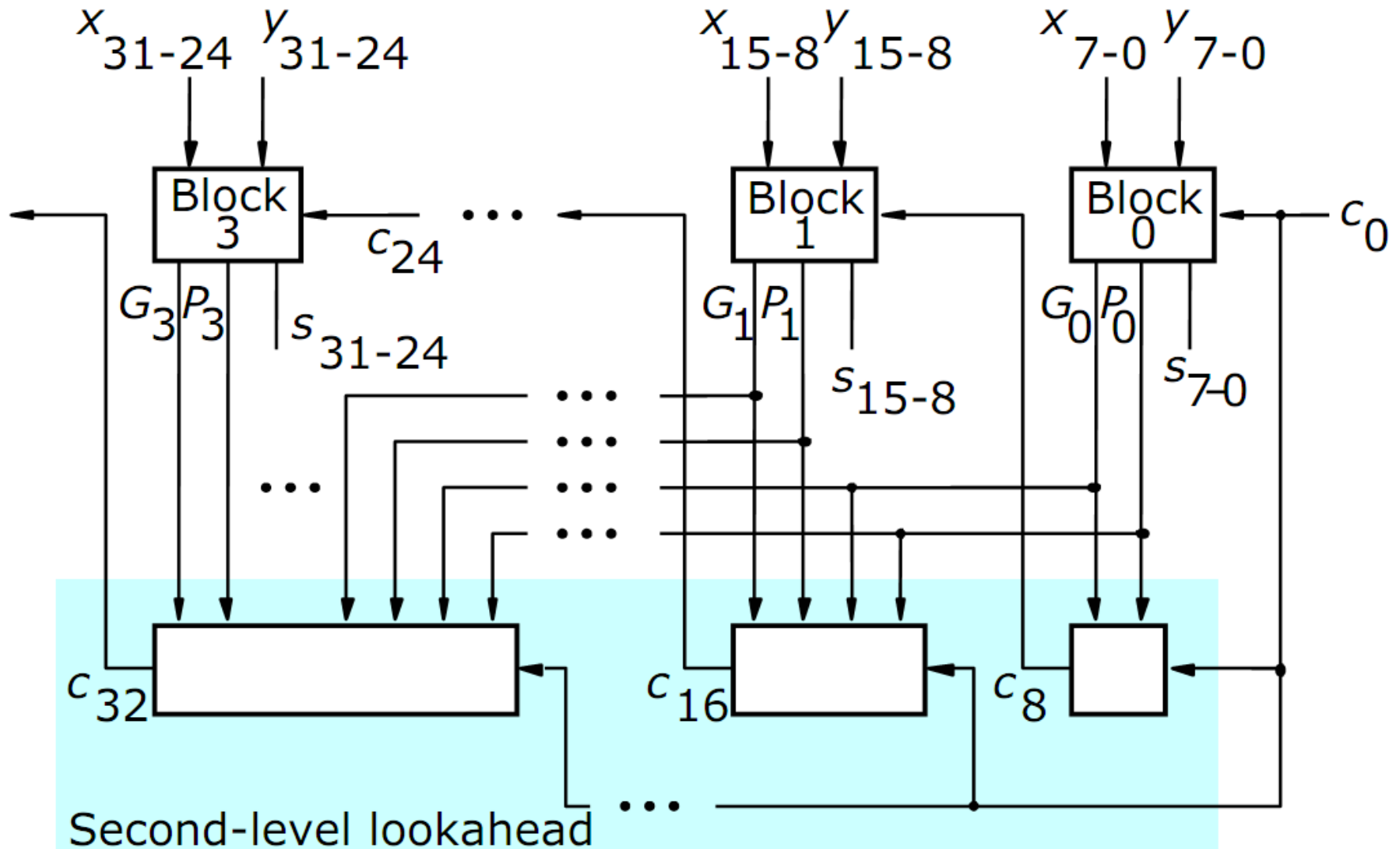

## Second level carry-lookahead circuit

- For the second level circuit:

$$P_0 = p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$$

$$G_0 = g_7 + p_7 g_6 + p_7 p_6 g_5 + \dots + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$

$$c_8 = G_0 + P_0 c_0$$

$$c_{16} = G_1 + P_1 c_8 = G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$



# Hierarchical CLA analysis

- Assuming a fan-in constraint of four inputs, the time to add two 32-bit numbers involves

$G_j$ , and  $P_j$  require three gate delays,  $C_8$ ,  $C_{16}$ , and  $C_{24}$  are available after **five gate delays**. The time needed to add two 32-bit numbers involves these five gate delays plus **two more** to produce the internal carries in blocks 1, 2, and 3, plus **one more gate delay** (XOR) to generate each sum bit. **This gives a total of eight gate delays.**